



# VIGNANA BHARATHI INSTITUTE OF TECHNOLOGY

(A UGC Autonomous Institution, Approved by AICTE, Accredited by NBA & NAAC-A Grade, Affiliated to JNTUH)

(Sponsored by Swamy Vivekananda Educational Trust)

Aushapur(V), Ghatkesar(M), MedchalDist, Telangana 501301

Marks


Roll No. : 22PGIAD4AD

Year/Semester : 1-1

Subject : ECA

Branch : ECE

Submission Date :


No : 1

Signature of the faculty member with date :

## Assignment Sheet

- 1) a) With the help of neat diagram & graphical representation explain the operation of class B power amplifier (push-pull configuration). Derive the expression for efficiency & calculate the value of maximum efficiency.

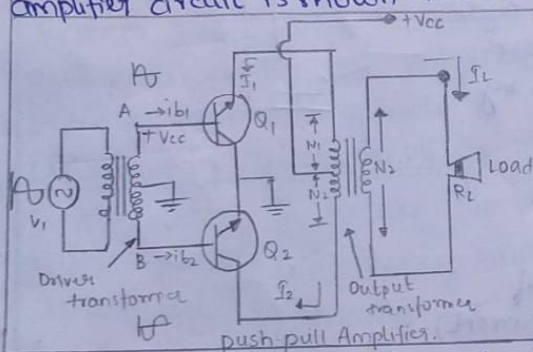A. The pushpull circuit requires two transformers, one as input transformer called driver transformer and other to connect the load called output transformer. The input signal is applied to the primary of the driver transformer. Both the transformers are centre tapped transformers. The push pull class B amplifier circuit is shown below



In the circuit,  $Q_1$  &  $Q_2$  are n-p-n type. The circuit can use both  $Q_1$  and  $Q_2$  of p-n-p type. In such a case, the only change is that the supply voltage must be  $-V_{cc}$ , the basic circuit remains the same. Generally the circuit using n-p-n transistors is used. Both the transistors are in common emitter configuration.

The driver transformer drives the ckt. The input signal is applied to the primary of

the driver transformer. The centre tap on the secondary of the driver transformer is grounded. The centre tap on the primary of the output transformer is connected to the supply voltage  $+V_{cc}$ .

With respect to the centre tap, for a +ve half cycle of input signal, the point A on the secondary of the driver transformer will be positive. While the point B will be negative. Thus the voltages in the two halves of the secondary of the driver transformer will be equal but with opposite polarity. Hence the input signals applied to the base of the transistors  $Q_1$  &  $Q_2$  will be  $180^\circ$  out of phase.

The transistor  $Q_1$  conducts for the positive half cycle of the input producing +ve half cycle across the load. While the transistor  $Q_2$  conducts for the -ve half cycle of the input producing -ve cycle across the load. Thus across the load, we get a full cycle for a full input cycle. The basic push pull operation

When point A is +ve, the transistor  $Q_1$  gets driven into an active region while, the transistor  $Q_2$  is in cut-off region. While when point A is -ve, the pt B is +ve, hence the  $Q_2$  gets into active &  $Q_1$  is in cut-off region.



OperationDc Operation

The dc biasing point i.e. Q point is adjusted on the x-axis such that  $V_{CEQ} = V_{CC}$  &  $I_{CEQ}$  is zero. The coordinate points for the Qpt are  $(V_{CC}, 0)$


Dc power  $I_p$ : Because each transistor Op is in the form of rectifier (half-wave) the peak value of current will be taken from dc value or average value. The dc value is taken as  $\frac{I_m}{\pi}$  &  $I_p/\pi$

$$I_{dc} = \frac{I_m}{\pi} + \frac{I_m}{\pi} \Rightarrow 2 \frac{I_m}{\pi} \quad \text{--- (1)}$$


Total dc power input

$$P_{dc} = V_{CC} \times I_{dc} = \left( \frac{2I_m}{\pi} \right) V_{CC} \quad \text{--- (2)}$$

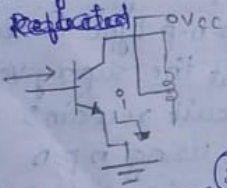Ac Operation When an Ac signal is applied to the driver transformer for +ve half cycle transistor  $Q_1$  conducts & the path of the current drawn by  $Q_1$  is given by



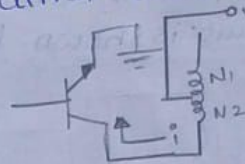2) Similarly for -ve half cycle path of the current drawn by transistor  $Q_2$  is given by



$$\Rightarrow R_L' = \frac{R_L}{n^2} \quad \text{where } n = \frac{N_2}{N_1} \quad \text{--- (3)}$$

$$\text{then } \frac{1}{R_L'} = \frac{I_m}{V_m} \Rightarrow R_L' = \frac{V_m}{I_m} \quad (I_m = \text{peak value of the collector current}) \quad \text{--- (4)}$$

Ac Power Output

As  $I_m$  &  $V_m$  are the peak values

$$V_{rms} = \frac{V_m}{\sqrt{2}} \quad \text{--- (5)}$$

$$I_{rms} = \frac{I_m}{\sqrt{2}} \quad \text{--- (6)}$$

$$P_{ac} = V_{rms} I_{rms} = I_{rms}^2 R_L' = \frac{V_{rms}^2}{R_L'} \quad \text{--- (7)}$$

$$P_{ac} = \frac{V_m I_m}{2} = \frac{I_m^2 R_L'}{2} = \frac{V_m^2}{2 R_L'} \quad \text{--- (8)}$$

$$\text{Efficiency } \% \eta = \frac{P_{ac}}{P_{dc}} \times 100 = \frac{\left( \frac{V_m I_m}{2} \right)}{\frac{2}{\pi} V_{CC} I_m} \times 100$$

$$\boxed{\% \eta = \frac{\pi}{4} \frac{V_m}{V_{CC}} \times 100} \quad \text{--- (9)}$$



### Maximum Efficiency


from eq (1), it is clear that as the peak value of the collector voltage  $V_m$  increases, the efficiency increases. The maximum value of  $V_m$  possible is equal to  $V_{CC}$  as shown

$$V_m = V_{CC} \text{ for maximum } \eta$$

$$\% \eta_{max} = \frac{\pi}{4} \times \frac{V_{CC}}{V_{CC}} \times 100$$

$$= 78.5\%$$

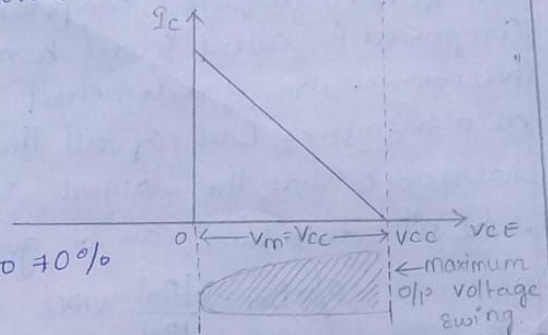for practical circuits it is up to 65 to 70%



b) Discuss about the distortion present in power amplifiers. Derive the expression for the total amount of distortion present in the amplifiers. Explain how even harmonic distortion can be reduced in a class B push-pull configured amplifier. Explain the origin of crossover distortion. Describe various methods to minimize the distortion.

- A) Distortion in Power Amplifiers The input signal applied to the amplifiers is alternating in nature. The basic features of any alternating signal are amplitude, frequency and phase. The amplifier output should be reproduced faithfully i.e. there should not be the change or distortion in the amplitude, frequency and phase of the signal. Hence the possible distortions in any amplifier are amplitude distortion, phase distortions and frequency distortion. But the phase distortions are not detectable by human ears as human ears are insensitive to the phase changes while the change in gain of the amplifier with respect to the frequency is called frequency distortions.

#### Harmonic distortion:

The Harmonic distortion means the presence of the frequency components in the output waveform, which are not present in the input signal. The component of the additional frequency components same as the input signal is called fundamental frequency component. The additional frequency components present in the output signal are having frequency components. These components are called harmonic components or harmonics.



For example, if the fundamental frequency of  $f$  Hz, then the output signals contains fundamental frequency component of  $f$  Hz & additional frequency components at  $2f$  Hz,  $3f$  Hz,  $4f$  Hz & so on. The  $2f$  component is called second harmonic, the  $3f$  component is called third harmonic. The fundamental frequency component is not considered as a harmonic. Out of all the harmonic components, the second harmonic has the largest amplitude.

→ The  $n^{\text{th}}$  distortion can be given as

$$\% D_n = \frac{|B_n|}{|B_1|} \times 100$$


for second harmonic  $\Rightarrow D_2 = \frac{B_2}{B_1} \times 100\%$

for 3rd harmonic  $\Rightarrow D_3 = \frac{B_3}{B_1} \times 100\%$

for total harmonic distortion can be as  $\% D = \sqrt{D_2^2 + D_3^2 + \dots} \times 100\%$
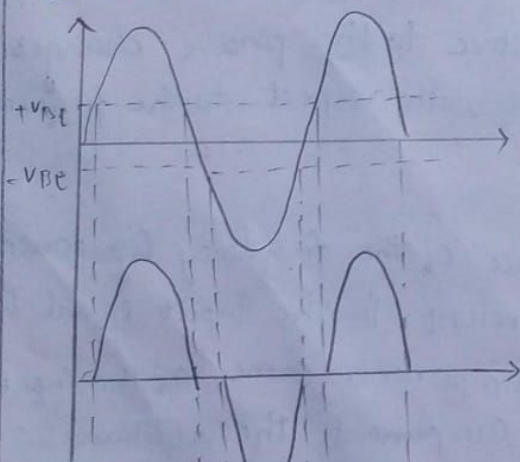
### Cross Over distortion:-

For a transistor to be in active region, the base emitter junction must be forward biased, this is done till the voltage applied becomes greater than cut in voltage ( $V_{BE}$ ), when the transition occurs from one transistor to the other transistor, if a second transistor is not going into conduction stage until it reaches cut in voltage the output waveform produces oval, this is called as cross-over distortion.



Cross-over distortion

### Elimination of cross-over distortion


→ To eliminate the cross-over distortion some modifications are necessary in the basic circuit of class B amplifiers. The basic reason for the cross over distortion is the cut-in voltage of the transistor junction. To overcome this cut-in voltage, a small forward biased is applied to the transistor.


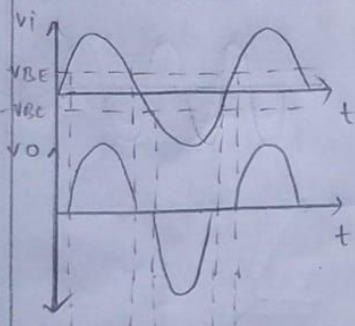
### Origin of cross-over distortion:

For a transistor to be in active region the base-emitter junction must be forward biased. The junction cannot be made forward biased till the voltage applied becomes greater than cut-in voltage ( $V_{BE}$ ) of the junction, which is generally 0.7V for silicon & 0.2V for germanium transistor. Hence as long as the magnitude of the input signal is less than the cut-in voltage of the base-emitter junction, the collector current remain zero & transistor remains in cut-off region.

Hence there is a period between the crossing of the half cycle of the input signal, for which none of the transistors is active and the output is zero. Hence the nature of the output signal gets distorted and no longer remains same as that of input. Such a distorted output wave form due to the cut-in voltage is the cross-over distortion. Such a distortion in the o/p signal is called as cross-over distortion.



### Methods to minimize the distortion

To minimize the distortion in power Amplifiers.

- 1) Choose the correct Amplifier class.
- 2) Linearization Techniques
- 3) Negative feedback
- 4) Component selection
- 5) proper biasing
- 6) Harmonic filtering
- 7) Optimized Grounding & layout

- ② A class B push-pull amplifier supplies power to a resistive load of  $12\Omega$ . The o/p transformer has a turns ratio of 3:1 and efficiency of 78.5%. Obtain
- a) Maximum power output
  - b) Maximum power dissipation in each transistor
  - c) Maximum base & collector current for each transistor
- Assume  $h_{fe} = 25$  &  $V_{CC} = 20V$ .

$$R_L = 12\Omega$$

$$\text{turns ratio} = \frac{n_1}{n_2}$$

Sol: Given  $R_L = 12 \Omega$

$$\text{Turns Ratio} = \frac{N_1}{N_2} = 3:1$$

$$\text{Efficiency } \eta = 78.5\%$$

$$h_{fe} = 25$$

$$V_{CC} = 20V$$

$$(i) P_{out} = \frac{V_m^2}{2R_L'} \quad (V_m = V_{CC}) \text{ at Maximum}$$

$$= \frac{V_{CC}^2}{2R_L'}$$

$$\text{where } R_L' = n^2 R_L$$

$$= \left(\frac{N_1}{N_2}\right)^2 R_L$$

$$= (3)^2 R_L$$

$$= (3)^2 \times 12$$

$$R_L' = 108 \Omega$$

$$= \frac{(20)^2}{2 \times (108)}$$

$$P_{out} = 1.85W$$

(ii) Max power dissipation

$$P_d(\max) = \frac{4}{\pi^2} P_o(ac)$$

$$= \frac{4}{(\pi)^2} (1.85)$$

$$P_d(\max) = 0.75W$$

$$P_d(\max) \text{ per transistor} = \frac{0.75}{2} = 0.375W$$

$$(iii) \text{Collector Current } I_c = \frac{P_{out}}{V_{CC}}$$

$$= \frac{1.85}{20} = 0.0925 A$$

$$0.0925 A$$



$$\text{Base Current} = I_b = \frac{I_c}{h_{fe}}$$


$$= \frac{0.0925}{25}$$

$$I_b = 0.0037 \text{ A}$$



③ With the help of neat diagram & graphical representation explain the Operation of class-A power amplifier. Derive the expression for efficiency and calculate the value of maximum efficiency

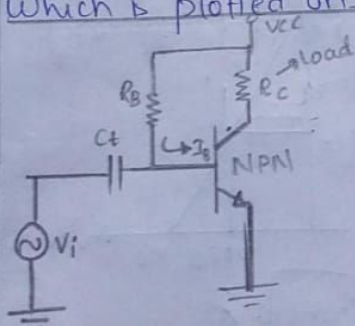A) Series Fed class-A power amplifier:-

→ For any amplifier Operating point (Q-pt) is fixed by selecting the proper DC Biasing to the transistor used. This Q-point is shown on the load line which is plotted on the Output characteristics of the transistor.



Series fed  
Class-A Amplifier

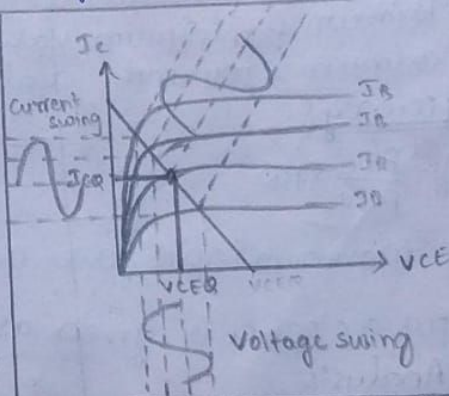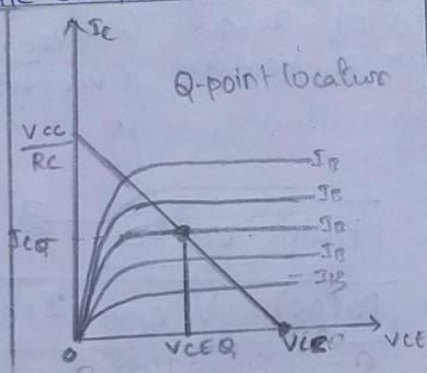

→ For a Class A amplifier Q-point is at the centre of the load line.

→ If the Q-point & the input signal are selected such that the output signal is obtained for a full input cycle (360°). For class A amplifiers the Q-point is at the centre of the loadline.

→ In series fed class-A Amplifier load resistance/resistor is directly connected to the output of the transistor.

→ Therefore, this is also called as direct coupled class-A amplifier.


→ In series fed class A amplifier the transistor is always in Active region.

→ When an input AC signal is applied, the output will vary from its DC biasing Operating voltage & current.

DC-Analysis For DC Analysis open circuit AC sources and capacitors

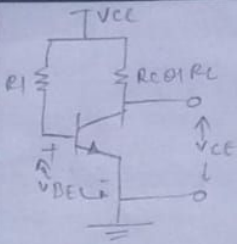→ The Q-point coordinates for the circuit  $V_{CEQ}, I_{CQ}$





→ Apply KVL for the loop base & emitter  $V_{CC} - I_B R_B - V_{BE} = 0$  — (1)

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} \quad (2)$$

$$I_C = \beta I_B \quad (3)$$

Apply KVL for the loop C & E loop  $V_{CC} - I_C R_C - V_{CE} = 0$  — (4)

$$V_{CE} = V_{CC} - I_C R_C \quad (5)$$

~~State~~ ⇒ To plot the dc load line we have to consider two worst case conditions for the given circuit

(i) When the transistor is in saturation region i.e.  $V_{CE} = 0$

then eq (5) becomes  $V_{CC} - I_C R_C = 0$

$$I_{CQ} = \frac{V_{CC}}{R_C} \quad (6)$$

(ii) When the transistor is in cut-off state i.e.  $I_C = 0$

then eq (5) becomes  $V_{CEQ} = V_{CC}$  — (7)

→ Maximum & minimum values of  $I_C$  are  $(V_{CC}/R_C, 0)$

→ Maximum & minimum value of  $V_{CE}$  are  $(V_{CC}, 0)$

### Efficiency

$$\eta = \frac{P_{ac}}{P_{dc}} \times 100\%$$

then maximum input power DC  $P_{i(dc)} = V_{CEQ} I_{CQ}$  — (8)

output ac power is given as  $P_{o(ac)} = V_{CE(rms)} I_{CQ(rms)}$  — (9)

### AC-Analysis

$$P_{o(ac)} = I_{CQ(rms)}^2 R_C \quad (10)$$

$$P_{ac} = \frac{V_{CE(rms)}^2}{R_C} \quad (11)$$

Generally  $V_{rms} = \frac{V_m}{\sqrt{2}}$  &  $I_{rms} = \frac{I_m}{\sqrt{2}}$


→ Similarly in terms of peak signal  $V_{rms} = \frac{V_p}{\sqrt{2}}$  &  $I_{rms} = \frac{I_p}{\sqrt{2}}$

→ In terms of peak to peak signal  $V_{rms} = \frac{V_{pp}}{2\sqrt{2}}$  &  $I_{rms} = \frac{I_{pp}}{2\sqrt{2}}$

Rewriting eq (9) with peak to peak values.

$$P_{o(ac)} = \frac{V_{CE(pp)}}{2\sqrt{2}} \times \frac{I_{C(pp)}}{2\sqrt{2}} \Rightarrow P_{o(ac)} = \frac{V_{CE(pp)} I_{C(pp)}}{(2\sqrt{2})(2\sqrt{2})}$$
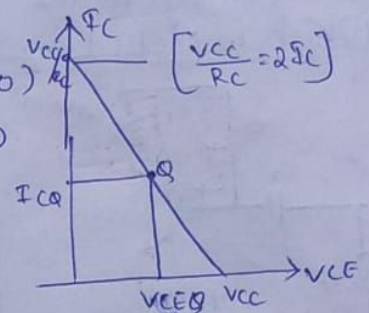
$$P_{o(ac)} = \frac{V_{CE(pp)} I_{C4pp}}{8}$$





(9)

In similar manner, rewriting (10) & (11) by substituting peak to peak voltage & current values

$$(11) \rightarrow P_{o(ac)} = \frac{I_c^2 (p-p) R_c}{(2\sqrt{2})^2} \Rightarrow \frac{I_c^2 (p-p) R_c}{8}$$

$$(12) \rightarrow P_{o(ac)} = \frac{V_{ce}^2 (p-p) R_c}{(2\sqrt{2})^2} \Rightarrow \frac{V_{ce}^2 (p-p) R_c}{8}$$

Efficiency:  $\eta = \frac{P_{ac}}{P_{dc}} \times 100\%$

$$\eta = \frac{V_{CEQ}(p-p) \cdot I_{CQ}(p-p)}{8 V_{CEQ} I_{CQ}} \Rightarrow \frac{(V_{CEmax} - V_{CEmin})(I_{Cmax} - I_{Cmin})}{8 V_{CEQ} I_{CQ}}$$

Maximum efficiency:

$$\left. \begin{array}{l} V_{max} = V_{cc} \text{ \& } V_{min} = 0 \\ I_{max} = 2 I_{CQ} \text{ \& } I_{min} = 0 \end{array} \right\} \text{ for maximum swing}$$

$$\% \eta = \frac{(V_{cc} - 0)(2 I_{CQ} - 0)}{8 V_{CC} \times I_{CQ}} \times 100$$

$$\% \eta = \frac{1}{4} \times 100$$

$$\boxed{\% \eta = 25\%} \rightarrow \text{maximum efficiency}$$

4) a) A single ended class A amplifier has a transformer coupled load of  $8 \Omega$ . If the transformer turns ratio is 10, Find the maximum power O/P delivered to the load. Take the zero signal collector current  $500 \text{ mA}$

Sol Given  $R_L = 8 \Omega$

$$\text{Turns Ratio: } \left( \frac{N_1}{N_2} \right) = 10:1$$

$$I_C = 500 \text{ mA} = I_m$$

Then Maximum power Output delivered is

$$P_{ac} = \frac{V_m^2}{2 R_L'}$$

$$\text{(where } V_m = I_m R_L')$$

$$= (500)(800 \Omega)$$

$$= (0.4)^2$$

$$(2)(800 \times 10^3)$$

$$V_m = 0.4 \text{ V}$$

$$\boxed{P_{ac} = 0.1 \text{ W}}$$

$$\begin{aligned} \text{where } R_L' &= n^2 R_L \\ &= (10)^2 \cdot 8 \\ &= 800 \Omega \end{aligned}$$



b) A transistor in a transformer coupled (Class-A) power amplifier has to deliver a maximum of 5 watts to a load of 4 $\Omega$  load. The quiescent point is adjusted for symmetrical swing, and the collector supply voltage  $V_{CC} = 20$  volts, Assume  $V_{min} = 0$  volts

(i) what is the transformer turns ratio.

(ii) what is the peak collector current

A) Given  $P_{max} = 5$  watts

$$R_L = 4\Omega$$

$$V_{CC} = 20 \text{ volts}$$

then  $V_{pp}$  or  $V_m$  =

$$\therefore P = \frac{V_m^2}{2R_L}$$

$$V_m = \sqrt{2 \cdot P \cdot R_L}$$

$$= \sqrt{2 \times 5 \times (4)}$$

$$\boxed{V_m = 6.32V}$$

$$(i) V_m = \frac{V_{CC}}{2N}$$

$$N = \frac{20}{2V_m}$$

$$N = \frac{20}{2 \times 6.32}$$

$$\boxed{N = 1.58 \text{ (turns ratio)}}$$

(ii) Peak collector current  $I_m$  or  $I_c$

$$V_m = I_{c \text{ peak}} \cdot R_L$$

$$6.32 = I_{c \text{ peak}} (4)$$


$$I_{c \text{ peak}} = \frac{6.32}{4}$$

$$\boxed{I_{c \text{ (peak)}} = 1.58 \text{ Amps}}$$




5) List possible Configurations of tuned Amplifiers.

A) b)

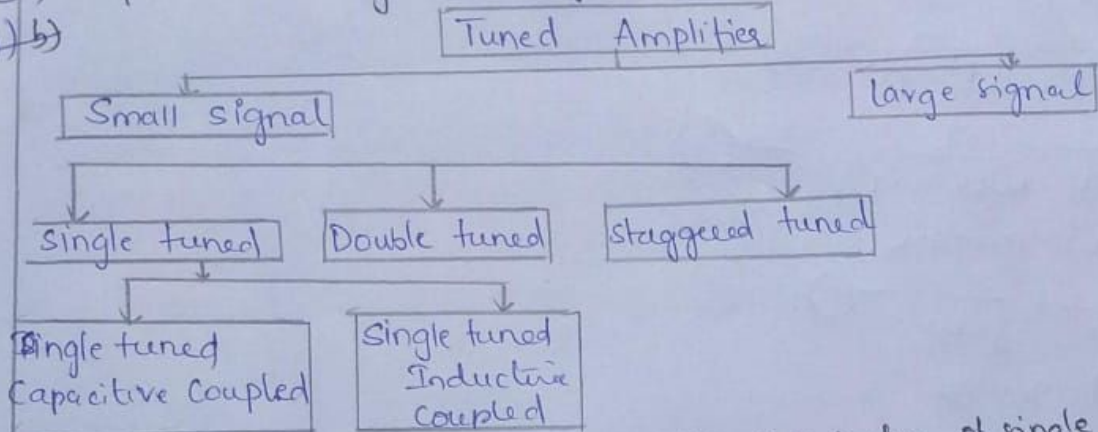

b) Derive the expression for Bandwidth & Q-factor of single tuned, capacitive coupled amplifiers. List the assumption made for the derivation

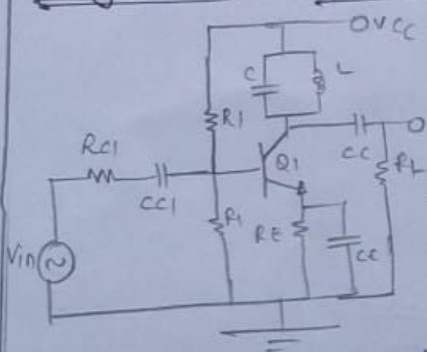
A) Single-tuned. Capacitive Coupled Amplifiers




L & C tuned circuit is not connected b/w collector & ground by the transistor will be short circuited at some frequency other than resonant frequency

⇒ Modified equivalent ckt using Miller's theorem  
 ⇒ According to Miller's theorem, the feedback capacitance  $C_c$  is  $C_c(1-A)$  on the i/p side and  $C_c(A-1/A)$  on the output side. But where as Resistance is  $r_{b'e}/(1-A)$  on i/p side  $r_{b'c}/(A-1/A)$  on

the output side

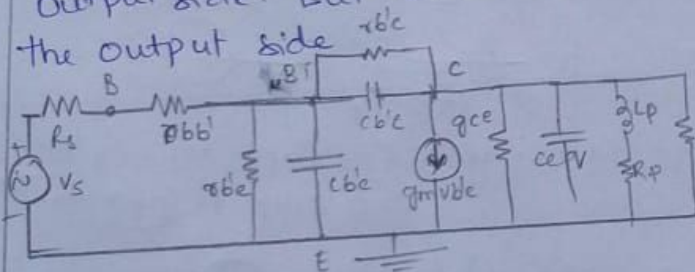

Hybrid-π Model

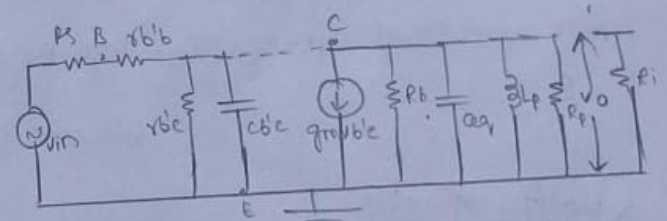

Simplified equivalent ckt

Series Admittance

$$Y_s = \frac{1}{R + j\omega L} \quad \text{--- (1)}$$

Ratio analyze the eq (1)

$$Y_s = \frac{1}{R + j\omega L} \times \frac{R - j\omega L}{R - j\omega L}$$

$$= \frac{R - j\omega L}{(R + j\omega L)(R - j\omega L)}$$

$$\Rightarrow \frac{R - j\omega L}{R^2 - (j\omega L)^2}$$

$$\Rightarrow \frac{R - j\omega L}{R^2 + (\omega L)^2}$$

$$\Rightarrow \frac{R - j\omega L}{R^2 + \omega^2 L^2}$$

$$= \frac{R}{R^2 + \omega^2 L^2} - \frac{j\omega L}{R^2 + \omega^2 L^2}$$



Now Multiply & divide with  $\omega$  in Complex form only

$$= \frac{R}{R^2 + \omega^2 L^2} - \left( \frac{j\omega L}{R^2 + \omega^2 L^2} \times \frac{\omega}{\omega} \right)$$

$$= \frac{R}{R^2 + \omega^2 L^2} - \frac{j\omega^2 L}{Rj(R^2 + \omega^2 L^2)} \quad \text{--- (2)}$$

Admittance in parallel

$$Y_p = \frac{1}{R_p} + \frac{1}{j\omega L_p} \quad \text{--- (3)}$$

from (2) & (3)  $Y_s = Y_p$

$$= \frac{1}{R_p} + \frac{1}{j\omega L_p}$$

Eq (3) can be written as

$$Y_s = \frac{1}{\frac{R^2 + \omega^2 L^2}{R}} + \frac{1}{\frac{j\omega(R^2 + \omega^2 L^2)}{\omega^2 L}}$$

$$\therefore R_p = \frac{R^2 + \omega^2 L^2}{R} \quad L_p = \frac{R^2 + \omega^2 L^2}{\omega^2 L} \quad \text{--- (4)}$$

At resonant frequency ( $\omega L \gg R$ ) then  $R_p = \frac{\omega^2 L^2}{R}$

At resonant frequency ( $\omega \gg R$ ) then  $L_p = L$

for resonant frequency to become  $f_r = \frac{1}{2\pi \sqrt{L_p C_{eq}}} \quad \text{--- (6)}$

where  $C_{eq} = C_o + C$  where  $C$  = capacitance of tuned ckt  
 $C_o$  = output capacitance

### Quality factor

$$Q = \frac{X_L}{R} \text{ which is also equal to } Q = \frac{\omega_r L_p}{R_p} \quad \text{--- (7)}$$

where  $\omega_r$  = angular frequency at resonance

$L_p$  &  $R_p$  are inductance & resistance of tank ckt

$\Rightarrow$  Quality factor can be written in 2-ways

1) Loaded Quality factor ( $Q_L$ ): when the ckt is connect to any external load in an amplifier //

$$Q_L = \frac{\text{max energy stored}}{\text{dissipated energy in tank ckt} + \text{dissipated energy due to external load}}$$

$$\boxed{Q_L = \frac{\omega_r L}{R_C}} \quad \text{--- (8)}$$



Unloaded Quality factor ( $Q_0$ ):- When the tank ckt of any amplifier is not connected to any load.

$$Q_u = \frac{\text{max energy stored per cycle}}{\text{energy dissipated per cycle in tank ckt}}$$

$$Q_u = \frac{\omega_r L}{R_o} \quad \text{--- (a)}$$

Bandwidth

$$\Delta f = \frac{1}{2\pi R_{eff} C_v}$$

$$= \frac{\omega_r}{2\pi Q_{eff}}$$

Quality factor


$$Q = \frac{f_o}{BW}$$

$f_o \Rightarrow$  resonant frequency

6) a) Using the circuit diagram and equivalent circuit of inductively Coupled single stage tuned amplifiers. Derive expression bandwidth which interrelated to the circuit components values and quality factor of the tuned circuit and resonant frequency.

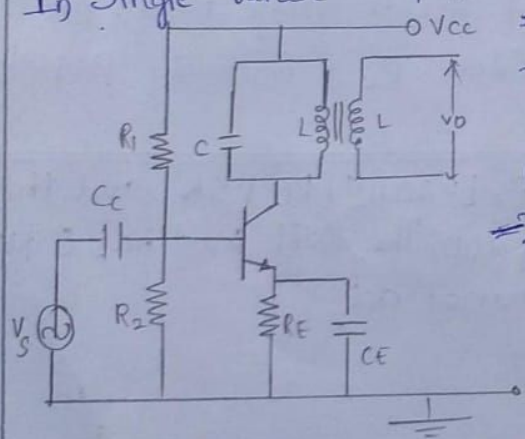A) Inductive Coupled Single Tuned Amplifiers:-

In Single tuned amplifiers, dc circuit is used for frequency tuning.  $\Rightarrow$  If the Output is taken across an inductor, then the tuned ckt is called inductively coupled tuned circuit. It is otherwise called as transformer coupled tuned ckt. &



$\Rightarrow$  The circuit typically consists of a tuned ckt connected in parallel with the load resistor  $R_L$ . The tuned ckt is coupled to the input and output circuits via mutual inductance  $M$ . The input signal is applied across the

tuned circuits, and the Output is taken across the load resistor  $R_L$ .

$\Rightarrow$  The resonant frequency  $\omega_0$  of the tuned ckt is given by

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$\Rightarrow$  The Quality factor  $Q$  of the tuned circuit is defined as the ratio of the energy stored in the circuit to the energy dissipated per radian at resonance. It is given by



$$Q = \frac{\omega_0 L}{R_{eq}}$$

Where  $R_{eq}$  is the equivalent Resistance of tuned ckt  
For the Bandwidth BW is related to the quality factor  $Q$  & the resonant frequency  $\omega_0$ .

$$BW = \frac{\omega_0}{Q}$$

→ For parallel resonant ckt, the equivalent Resistance  $R_{eq}$  seen by the inductor is equal to the resistance parallel with inductor.  
In this it's  $R_L$  ✓

thus, the Quality factor  $Q$  is expressed as

$$Q = \frac{\omega_0 L}{R_L}$$

Substituting in Bandwidth formula we get

$$BW = \frac{\omega_0}{\frac{\omega_0 L}{R_L}}$$

$$\boxed{BW = \frac{R_L}{L}}$$

So the BW of the inductively coupled single-stage tuned Amplifier is directly proportional to the load Resistance  $R_L$  & inversely proportional to the inductance  $L$ .

b) In a tuned Amplifier ckt  $C = 500\text{pF}$ ,  $L = 20\mu\text{H}$ ,  $R_L = 1.5\text{k}$  and the transistor has  $h_{fe} = 50$  & i/p resistance of  $200$ . The coil used has  $Q$ -factor 30.  
Calculate (i) resonant frequency of the tuned ckt.

(ii) Impedance of the tuned ckt  
(iii) Voltage gain of the stage

A) (i)  ~~$f_0 = \frac{1}{2\pi\sqrt{LC}}$~~   $f_0 = \frac{1}{2\pi\sqrt{LC}}$

$$= \frac{1}{2\pi\sqrt{(500 \times 10^{-12})(20 \times 10^{-6})}}$$

$$f_0 = \frac{1}{2\pi\sqrt{10000 \times 10^{-12} \times 10^{-6}}}$$

$$= \frac{1}{2\pi\sqrt{10^{-14}}}$$



$$f_0 = \frac{1}{2\pi(10^{-7})}$$

$$= \frac{1}{6.28(10^{-7})}$$

$$\boxed{f_0 = 1.592 \text{ MHz}}$$

(ii) Impedance of the tuned ckt

$$Z = \sqrt{R_L^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

where  $\omega = 2\pi f_0$

$$\omega = 2 \times 3.14 \times 1.592 \times 10^6$$

$$\omega = 9.99 \times 10^6 \text{ rad/s}$$

$$Z = \sqrt{R_L^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

$$= \sqrt{(1.5 \times 10^3)^2 + \left(9.99 \times 10^6 \times 20 \times 10^{-6} - \frac{1}{9.99 \times 10^6 \times 500 \times 10^{-12}}\right)^2}$$

$$= \sqrt{(1.5 \times 10^3)^2 + (1998 - 200.2)^2}$$

$$= \sqrt{(1.5 \times 10^3)^2 + (-0.4)^2}$$

$$= \sqrt{2250000 + (0.16)}$$

$$= \sqrt{2250000.16}$$

$$\boxed{Z = 1500.00 \Omega}$$

iii) Voltage gain ( $A_v$ )

$$A_v = -h_{fe} \times \frac{Z}{R_L + R_{in}}$$

$$= -50 \times \frac{1500.0}{1500 + 200}$$

$$A_v = -44.117$$

$\therefore$  The Voltage gain of the stage is approximately

$$\boxed{A_v = -44.12}$$




7) a) Draw the circuit of double tuned transformer coupled amplifier and the working of it in detail and discuss the nature of the amplifier for different values of  $kQ=1$ ,  $kQ>1$ , and  $kQ<1$

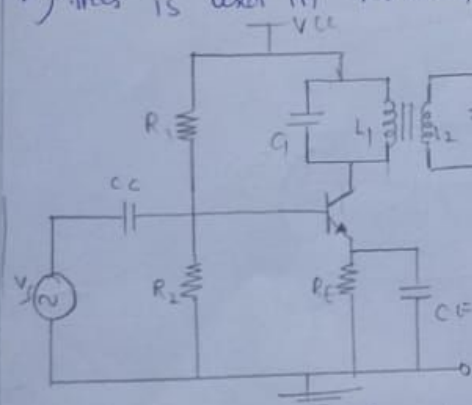A) To Overcome the drawback of single tuned amplifier, double tuned amplifiers are used. In this method, two tuned circuits are inductively coupled to each other.  $L_1C_1$  is used as collector load and  $L_2C_2$  is used as output circuit.  $R_1, R_2, R_E$  provide dc current and voltage for the transistor.

→ This circuit provides high impedance to the input signal and a large output appears across the tuned circuit  $L_1C_1$ . This output is inductively coupled to  $L_2C_2$  tuned circuit.

→ This is used in radio & television receiver.



Operation:

→ The signal which has to be amplified is a high-frequency signal and it is given to the i/p of the amplifier. The primary tuning circuit like  $L_1C_1$  can be tuned towards the i/p signal frequency.

→ In this state, the tuned circuit gives high reactance towards the signal frequency. As a result, huge o/p becomes visible at the o/p of the primary tuned circuit. Then it is coupled with the secondary tuned circuit like  $L_2C_2$  using mutual inductance. These circuits are widely used to connect different circuits of TV and radio receivers.

Nature of the amplifier

at  $kQ=1$  ⇒ when  $k=\frac{1}{Q}$ ,  $f_1=f_2=f_r$ . This condition is known as critical coupling.

$kQ<1$  ⇒ when  $k<\frac{1}{Q}$ , the peak gain is less than maximum gain and the coupling is poor.

$kQ>1$  ⇒ when  $k>\frac{1}{Q}$ , the circuit is overcoupled and response shows the double peak. Such double peak response is useful when more bandwidth is required.



b) Why Cascaded amplifiers are preferred for tuned amplifiers derive the BW effect formula for single tuned cascaded amplifiers (Synchronous)

### A) Effect of Cascading Single tuned Amplifier on Bandwidth:

In order to obtain a high overall gain, several identical stages of tuned amplifiers can be used in cascade. The Overall gain is the product of the voltage gains of the individual stages. Let us see the effect of cascading of stages on bandwidth.

Consider  $n$  stages of single tuned direct coupled amplifiers connected in cascade. We know that the relative gain of a single tuned amplifier with respect to the gain at resonant frequency  $f_r$  is

$$\left| \frac{A_v}{A_v(\text{at resonance})} \right| = \frac{1}{\sqrt{1 + (2sQ_{eff})^2}} \quad \text{--- (1)}$$

$\therefore$  the relative gain of  $n$  stage cascaded amplifiers becomes

$$\left| \frac{A_v}{A_v(\text{at resonance})} \right|^n = \left[ \frac{1}{\sqrt{1 + (2sQ_{eff})^2}} \right]^n = \frac{1}{[1 + (2sQ_{eff})^2]^{n/2}} \quad \text{--- (2)}$$

The 3 dB frequency for the  $n$  stage cascaded amplifier can be found by equating

$$\left| \frac{A_v}{A_v(\text{at resonance})} \right|^n = \frac{1}{\sqrt{2}}$$

$$\left| \frac{A_v}{A_v(\text{at resonance})} \right|^n = \frac{1}{(2)^{1/2}} \quad \text{--- (3)}$$

$$\text{eq (2) \& (3)} \quad [1 + (2sQ_{eff})^2]^{n/2} = (2)^{1/2}$$

$$[1 + (2sQ_{eff})^2]^n = 2$$

$$(1 + 2sQ_{eff})^2 = 2^{1/n}$$

$$(2sQ_{eff})^2 = 2^{1/n} - 1$$

$$2sQ_{eff} = \sqrt{2^{1/n} - 1} \quad \text{--- (4)}$$

$s \Rightarrow$  fractional variation

$$s = \frac{\omega - \omega_r}{\omega_r} = \frac{f - f_r}{f_r} \quad \text{--- (5)}$$

Substitute (5) in (4)



$$2 \left[ \frac{f - f_r}{f_r} \right] Q_{eff} = \pm \sqrt{2^{1/n} - 1}$$

$$2(f - f_r) Q_{eff} = \pm f_r \sqrt{2^{1/n} - 1}$$

$$\left[ f - f_r = \pm \frac{f_r}{2 Q_{eff}} \sqrt{2^{1/n} - 1} \right] \text{--- (6)}$$

Now consider  $f_1$  &  $f_2$  are lower & upper cut-off 3dB frequency

$$f_2 - f_r = + \frac{f_r}{2 Q_{eff}} \sqrt{2^{1/n} - 1} \text{--- (7)}$$

$$f_r - f_1 = + \frac{f_r}{2 Q_{eff}} \sqrt{2^{1/n} - 1} \text{--- (8)}$$

$f_r \Rightarrow$  resonant frequency

$f_2 \Rightarrow$  upper cut off frequency

$f_1 \Rightarrow$  lower cut off frequency

Adding (7) & (8)

$$f_2 - f_1 \Rightarrow (f_2 - f_1)_n = \frac{2 f_r}{\sqrt{2^{1/n} - 1}}$$

$$\boxed{(Bw)_n = Bw_1 \sqrt{2^{1/n} - 1}} \text{---}$$

$Bw_1 \rightarrow$  Bandwidth of single stage

$Bw_n \rightarrow$  Bandwidth of  $n$  stages


- (8) What is stagger tuning amplifier explain the circuit operation? Mention the need for stagger-tuned amplifiers with applications, advantages & disadvantages.

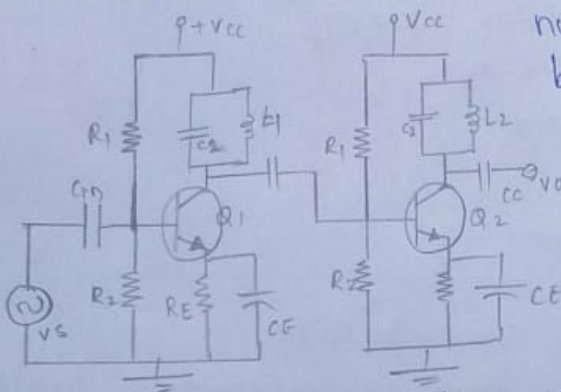A) Stagger tuned amplifier: In order to increase bandwidth, double tuned amplifiers are preferred, but their alignment is difficult. A much better overall response can be had by stagger tuning. If two or more tuned circuits are cascaded and tuned to the same frequency, it is called the synchronous tuning. The overall bandwidth is reduced. On the other hand, if the tuned circuits are cascaded and they are tuned to different frequency, it is possible to have increased with more desirable characteristics (i.e., flat passband with steeper sides). This technique

Operation A two stage tuned voltage amplifiers. In stagger tuned circuits two single tuned cascaded amplifiers having a certain bandwidth are taken and the resonant frequencies of the two tuned circuits are so adjusted that they are separated by an amount equal to the bandwidth of each stage. Stagger tuned amplifiers are usually designed so that the overall response exhibits maximum flatness around the center frequency  $f_0$ .



It needs a number of tuned circuits operating in union. If more number of stages are employed flatter will be the passband and steeper will be the gain fall outside the passband. Because of stagger tuning there is a loss of voltage gain. The overall frequency response of a stagger tuned amplifier is obtained by adding



individual response together. Since the resonant frequencies of different tuned circuits are displaced or staggered, they are referred as stagger tuned circuits.

Need for stagger-tuned circuits:

Wider Bandwidth: By using multiple tuned circuits with slightly different resonant frequencies, stagger-tuned amplifiers can achieve a broader bandwidth compared to single-tuned amplifiers. This wider bandwidth allows the amplifier to amplify a range of frequencies without significant loss of signal strength.

Improved selectivity: Stagger tuning can also improve the selectivity of the amplifier, allowing it to amplify specific frequency ranges while attenuating others. This is particularly useful in communication systems where signals from different channels need to be separated.

Reduced signal distortion: Stagger tuning can help reduce signal distortion by minimizing the interaction between adjacent stages in the amplifier. This can lead to cleaner amplification of the input signal.

Enhanced stability: Stagger-tuned amplifiers can be more stable over temperature and component variations compared to single-tuned amplifiers, providing more consistent performance over a range of operating conditions.

Applications of stagger tuned amplifier

- 1) These type of tuned amplifiers are employed in wideband applications for the amplifications of video.
- 2) IF amplifiers in the superheterodyne receiver.
- 3) TV receiver & satellite transponder.
- 4) Used in Wireless local area networks (WLANs).

- 5) Used in RF amplifier for radio applications like radio receivers.
- 6) Used for V-amplifiers for Oscilloscope working
- 7) Used in Various industrial applications
- 8) Used in radio VHF relay system

### Advantages

The stagger tuned amplifier advantages are

- 1) The tuning of this amplifier is very easy
- 2) It has better flat wideband characteristics.
- 3) The bandwidth is increased  $\sqrt{2}$  times when compared to single tuned amplifier.
- 4) The overall gain is increased due to the cascading of two single tuned amplifiers.
- 5) Enhanced stability of the circuit

### Disadvantages:

The stagger tuned amplifier disadvantages are

- 1) The alignment of staggs.-tuned amplifiers are difficult. Hence, two single tuned amplifiers are cascaded.
- 2) The selectivity is reduced and the tuning of tank ckt is critical.